

PHILIPS

LABORATORY REPORT

ELECTRON TUBES
SEMICONDUCTORS
COMPONENTS
MATERIALS

Group : Electronic Application Laboratory
F.A.P.E.S.A.,
Buenos Aires.
Date : August 25th 1961.
Author : L. Garlatti.
Title : Single-ended transformerless amplifier.
Ref.no.: IL/6127 EL.
Rep.no.: AR 6107.

PHILIPS ELECTRON TUBE DIVISION
INDUSTRIAL COMPONENTS AND MATERIALS DIVISION

VHR
29
oor de Historie v/d Radic

AR 6107

ELECTRONIC APPLICATIONS LABORATORY
E. A. P. E. S. A. BUENOS AIRES

GROUP: Radio
AUTHOR: L. Carlatti
TITLE: Single-ended transformerless amplifier
DATE: August 25th. 1961
REF: IL/6127 E1

S U M M A R Y

This report describes a transformerless amplifier for a gramophone using two 6C74 in Class B. The power output is 300 mW.

Published in English and Spanish

GENERAL CONSIDERATIONS:

The use of output transistors connected as either push-pull or asymmetric push-pull amplifiers is possible its direct coupling to low impedance speakers.

Symmetrical P.P. $Z_o = 4 V_B / I_c$

Asymmetrical P.P. $Z_o = \frac{V_B}{2} / I_c$

On the other hand, not being the optimum load value critical referred to the energy transference, it is possible to use speakers whose impedance differs of the estimated optimum value (logically, if we reduce the value of Z_o the efficiency of the stage will be lower on account of the greater consumption). In our case, we have followed the previous judgement using conventional speakers with a 5ohms impedance and a battery voltage of 9 V.

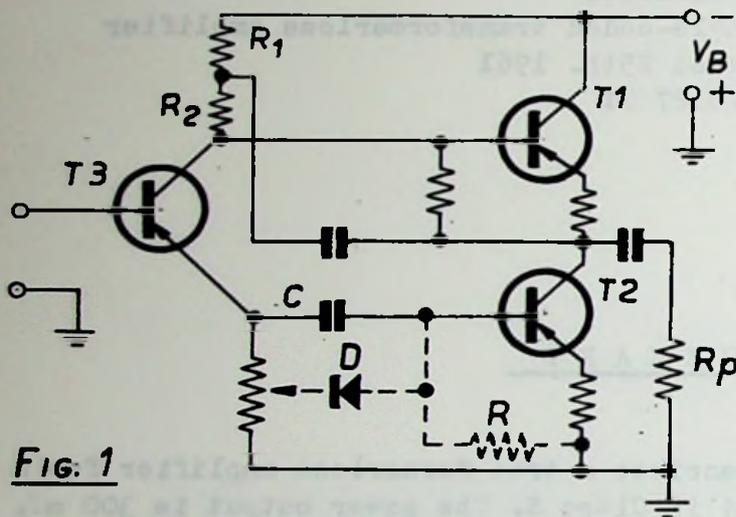


FIG. 1

In Fig. 1 is shown the output stage wiring. Transistor T3 drives transistor T1 using direct coupling between collector and base. The injected signal is taken from the ends of resistor R2. It must be remembered that under this conditions the speaker impedance will be in parallel with resistor R1. to avoid an excessive loss of signal it must be complied that $R1 \gg R_p$. (On the other hand, an excessive value of R1 will limit the maximum signal swing between collector and emitter of T3).

The driving signal for transistor T2 is taken from the emitter of transistor T3. As the output stage operates in Class B, when the transistor T2 is not conducting, capacitor C must discharge quickly during that half cycle. For this reason a divider has been introduced, formed by diode D and resistor R that also makes possible to fix the operating point of T2.

In the final circuit two preamplifier stages have been incorporated using transistors OC75 and a feedback loop has been included (capacitor C5) from collector to base of transistor T3.

Herewith are presented the measurements carried out on a prototype

Static measurements:

Este libro, no podrá ser copiado total ni parcialmente, como el
 respecto serán transmitidas a terceros, informaciones, conce-
 piones a los mismos. En caso de contravención, la F.A.P.E.S.A.
 promoverá contra quien resulte responsable, las acciones
 legales y criminales que correspondan en derecho.

A
B
C
D
E
F
G
H
I
J
K
L
M
N
P
Q
R
S
T
U
V
W
X
Y
Z

<u>Transistor</u>	OC75	OC75	OC75	2-OC74
I. Collector	1. mA.	2,4mA.	11mA.	10mA.
W. Collector and ground	0,9 V	1,15V.	1,7V.	0V.

Dynamic measurements:

Power output: 300 mW. with 5% harmonic distortion
 Sensivity at maximum output: 180mV.
 Frequency response: 50-4000 c/s (for -3dB)
 Total no-signal consumption: 27mA.
 Total maximum signal consumption: 115mA.

Conclusion:

The circuit employed provides a compromise solution in the case of not using transformers. However, it presents the disadvantage of the higher consumption and of using components that must have stricter tolerances due to the direct coupling.

References:

- 1) Single Ended Amplifier for Class B operation. H.C. Lin and B. White (Electronics May 29, 1955).

Report N°2/55 (W5502A.).

Handbook of Semiconductos Electronics, Lloyd P. Hunter.

Malaspina

Prepared by: C. Malaspina

Garlatti

Ing. L. Garlatti
 In charge of Radio Group
 E.A.L.

W. Feruglio

Ing. Walter Feruglio
 Chief Laboratory

--

Jamoco serán transmitidas e terceros, informaciones, conser-
 nencia a los mismos. En caso de contención, la FAPUSA
 promoverá contra quien resulte responsable, las acciones
 civiles y criminales que correspondan en derecho.



LIST OF MATERIALS

RESISTORS

- R₁ : 200 K $\frac{1}{2}W \pm 10\%$
- R₂ : 50K Potenciometer. Logar. Variat.
- R₃ : 27K $\frac{1}{2}W \pm 10\%$
- R₄ : 10 Ω " "
- R₅ : 3K3 " "
- R₆ : 27K " "
- R₇ : 2K7 " "
- R₈ : 10 Ω " "
- R₉ : 220 Ω " "
- R₁₀ : 10K " "
- R₁₁ : 10K " "
- R₁₂ : 180 Ω " 5%
- R₁₃ : 150 Ω " "
- R₁₄ : 100 Ω " "
- R₁₅ : 68 Ω " "
- R₁₆ : 100 Ω " 10%
- R₁₇ : 100 Ω " "
- R₁₈ : 0,5 Copper wire
- R₁₉ : 0,5 " "

CAPACITORS

- C₁ : 100 $\mu F \times 16V.$
- C₂ : 3,2 $\mu F \times 16V.$
- C₃ : 3,2 $\mu F \times 16V.$
- C₄ : 3,2 $\mu F \times 16V.$
- C₅ : 10K $\times 125V.$ (Polliester)
- C₆ : 100 $\mu F \times 16V.$
- C₇ : 100 $\mu F \times 16V.$
- C₈ : 1000 $\mu F \times 16V$


MISCELLANEOUS

- 1 - 2-0C74 transistor with heat sink.
- 1 - 0C79 transistor with heat sink
Code 56.200
- 2 - 0C75 Transistor
- 1 - 0A81 diode
- 1 - 5 Ω Loudspeaker

Este documento es propiedad de la FABRICA ARGENTINA DE PRODUCTOS ELECTRICOS S.A. y no puede ser copiado, reproducido o transmitido en forma alguna sin el consentimiento escrito de la misma. En caso de contravención, la F.A.P.E.S.A. promoverá acciones legales correspondientes.

A
B
C
D
E
F
G
H
I
J
K
L
M
N
O
P
Q
R
S
T
U
V
W
X
Y
Z

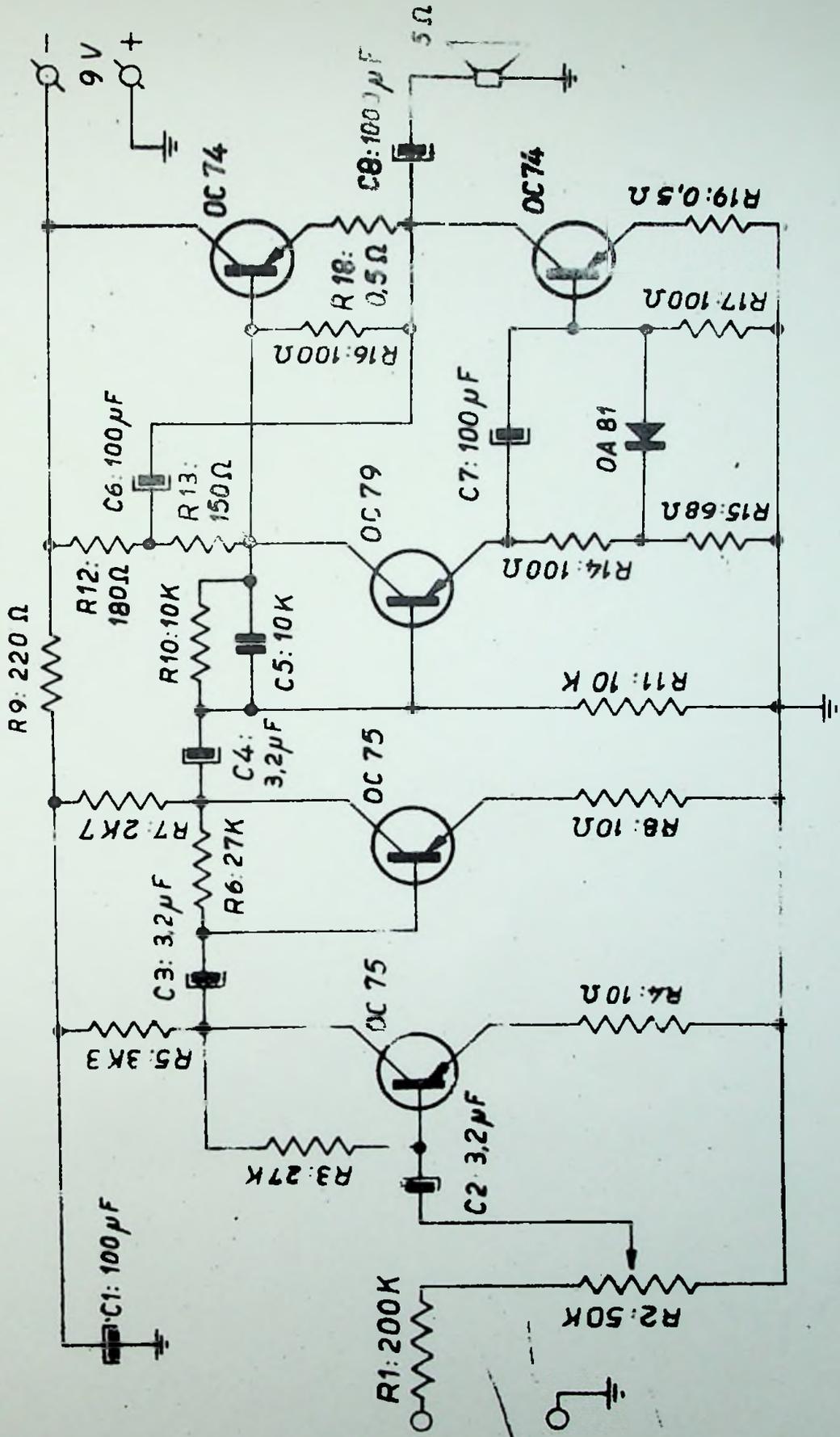Se reserva todos los derechos de propiedad intelectual y moral. En caso de reproducción, la F.A.P.E.S.A. promoverá contra quien resulte responsable, las acciones legales y judiciales que correspondan en derecho.



FABRICA ARGENTINA
DE PRODUCTOS ELECTRICOS
SOCIEDAD ANONIMA

Hojas	Reemplaza
	Hoja
	Fecha